

Name: <u>Umair Nadeem</u>	EE-272L Digital Systems Design
Reg. No.: <u>2023-EE-115</u>	Marks Obtained: _____

## Lab Manual

### Experiment 4

### Combinational Circuit Design: RGB LED using K-Maps

#### DSD Lab Manual Evaluation Rubrics

Assessment	Total Marks	Marks Obtained	0-30%	30-60%	70-100%
Code Organization (CLO1)	3		No Proper Indentation and descriptive naming, no code organization.  Zero to Some understanding but not working	Proper Indentation or descriptive naming or code organization.  Mild to Complete understanding but not working	Proper Indentation and descriptive naming, code organization.  Complete understanding, and proper working
Simulation (CLO2)	5		Simulation not done or incorrect, without any understanding of waveforms	Working simulation with errors, don't cares's(x) and high impedance(z), partial understanding of waveforms	Working simulation without any errors, etc and complete understanding of waveforms
FPGA (CLO2)	2		Not implemented on FPGA and questions related to synthesis and implementation not answered.	Correctly Implemented on FPGA or questions related to synthesis and implementation answered.	Correctly Implemented on FPGA and questions related to synthesis and implementation answered.

## TASKS:

### a. Truth Table of the Circuit:

$a[1]$	$a[0]$	$b[1]$	$b[0]$	$a > b$ <i>Purple</i>	$a = b$ <i>Yellow</i>	$a < b$ <i>Cyan</i>	<i>Red</i>	<i>Green</i>	<i>Blue</i>
0	0	0	0	0	1	0	1	1	0
0	0	0	1	0	0	1	0	1	1
0	0	1	0	0	0	1	0	1	1
0	0	1	1	0	0	1	0	1	1
0	1	0	0	1	0	0	1	0	1
0	1	0	1	0	1	0	1	1	0
0	1	1	0	0	0	1	0	1	1
0	1	1	1	0	0	1	0	1	1
1	0	0	0	1	0	0	1	0	1
1	0	0	1	1	0	0	1	0	1
1	0	1	0	0	1	0	1	1	0
1	0	1	1	0	0	1	0	1	1
1	1	0	0	1	0	0	1	0	1
1	1	0	1	1	0	0	1	0	1
1	1	1	0	1	0	0	1	0	1
1	1	1	1	0	1	0	1	1	0

### b. K-map:

#### 1. RED

$a[1] \ a[0] \setminus b[1] \ b[0]$	00	01	11	10
00	1	0	0	0
01	1	1	0	0
11	1	1	1	1
10	1	1	0	1

Equation using essential prime implicants:

$$\text{red} = (\sim b1 \ \& \ \sim b0) \mid (a0 \ \& \ \sim b1) \mid (a1 \ \& \ \sim b1) \mid (a1 \ \& \ a0) \mid (a1 \ \& \ \sim b0)$$

#### 2. GREEN

$a[1] \ a[0] \setminus b[1] \ b[0]$	00	01	11	10
00	1	1	1	1
01	0	1	1	1
11	0	0	1	0
10	0	0	1	1

Equation using essential prime implicants:

$$\text{green} = (\sim a1 \ \& \ \sim a0) \mid (b1 \ \& \ b0) \mid (\sim a1 \ \& \ b0) \mid (\sim a1 \ \& \ b1) \mid (\sim a0 \ \& \ b1)$$

### 3. BLUE


$a[1] \ a[0] \setminus b[1] \ b[0]$	00	01	11	10
00	0	1	1	1
01	1	0	1	1
11	1	1	0	1
10	1	1	1	0

Equation using essential prime implicants:


$$\text{blue} = (a1 \wedge b1) \vee (a0 \wedge b0)$$

#### c. Circuit Diagram using K-Map Equations:


**RED:**

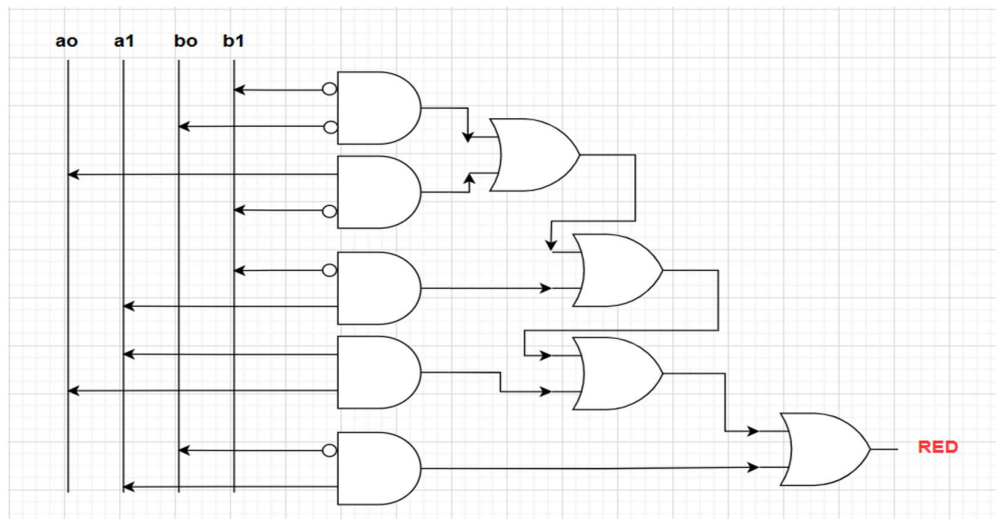


**BLUE:**

 

## GREEN:

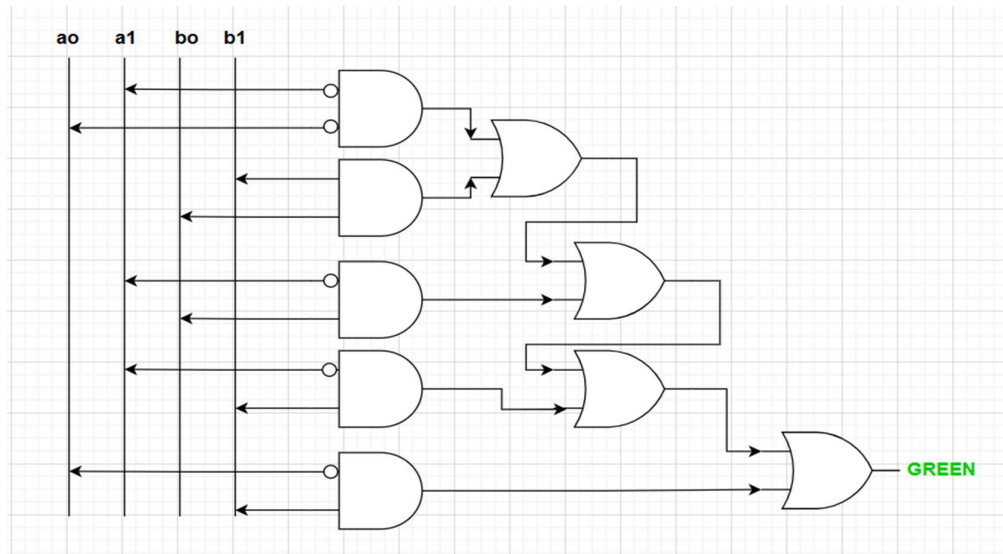

## d. Circuit diagram:

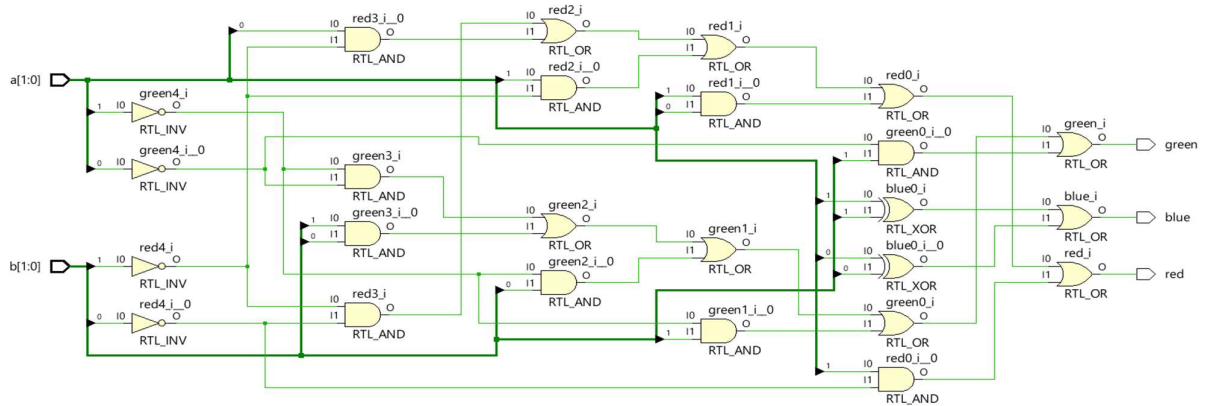

## e. Combinational Delay:

Combinational Delays					
From Port	To Port	Max Delay	Max Process Corner	Min Delay	Min Process Corner
<input checked="" type="checkbox"/> a[0]	<input checked="" type="checkbox"/> blue	9.175	SLOW	2.819	FAST
<input checked="" type="checkbox"/> a[0]	<input checked="" type="checkbox"/> green	8.819	SLOW	2.624	FAST
<input checked="" type="checkbox"/> a[0]	<input checked="" type="checkbox"/> red	8.981	SLOW	2.707	FAST
<input checked="" type="checkbox"/> a[1]	<input checked="" type="checkbox"/> blue	8.451	SLOW	2.551	FAST
<input checked="" type="checkbox"/> a[1]	<input checked="" type="checkbox"/> green	8.059	SLOW	2.363	FAST
<input checked="" type="checkbox"/> a[1]	<input checked="" type="checkbox"/> red	8.255	SLOW	2.442	FAST
<input checked="" type="checkbox"/> b[0]	<input checked="" type="checkbox"/> blue	9.001	SLOW	2.746	FAST
<input checked="" type="checkbox"/> b[0]	<input checked="" type="checkbox"/> green	8.653	SLOW	2.564	FAST
<input checked="" type="checkbox"/> b[0]	<input checked="" type="checkbox"/> red	8.817	SLOW	2.649	FAST
<input checked="" type="checkbox"/> b[1]	<input checked="" type="checkbox"/> blue	9.311	SLOW	2.911	FAST
<input checked="" type="checkbox"/> b[1]	<input checked="" type="checkbox"/> green	9.052	SLOW	2.751	FAST
<input checked="" type="checkbox"/> b[1]	<input checked="" type="checkbox"/> red	9.216	SLOW	2.831	FAST

Maximum Combinational delay is from b[1] to blue which is 9.311 ns.

## f. Resource Utilization:

The number of **LUTs utilized** is **2**, and the number of **IO ports utilized** is **7**

### 1. Slice Logic

Site Type	Used	Fixed	Available	Util%
Slice LUTs*	2	0	63400	<0.01
LUT as Logic	2	0	63400	<0.01
LUT as Memory	0	0	19000	0.00
Slice Registers	0	0	126800	0.00
Register as Flip Flop	0	0	126800	0.00
Register as Latch	0	0	126800	0.00
F7 Muxes	0	0	31700	0.00
F8 Muxes	0	0	15850	0.00

### 4. IO and GT Specific

Site Type	Used	Fixed	Available	Util%
Bonded IOB	7	0	210	3.33
Bonded IPADs	0	0	2	0.00
PHY_CONTROL	0	0	6	0.00
PHASER_REF	0	0	6	0.00
OUT_FIFO	0	0	24	0.00
IN_FIFO	0	0	24	0.00
IDELAYCTRL	0	0	6	0.00
IBUFDS	0	0	202	0.00
PHASER_OUT/PHASER_OUT_PHY	0	0	24	0.00
PHASER_IN/PHASER_IN_PHY	0	0	24	0.00
IDELAYE2/IDELAYE2_FINEDELAY	0	0	300	0.00
ILOGIC	0	0	210	0.00
OLOGIC	0	0	210	0.00